

**CSE/EEE120**  
**Final Exam**

Name: \_\_\_\_\_ ASU ID: \_\_\_\_\_

You have 1 hour and 50 minutes to complete and turn in this quiz (allow approximately 30 minutes for the multiple choice questions). Please read questions carefully and provide the answers in the form requested. SHOW YOUR WORK. Good luck!

---

1. Given the truth table for function  $f$ , answer the questions below (4 points each, 40 points total):

Line#	a	b	c	f
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	1
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

- (a) Write function  $f$  in the canonical SOP and POS forms.

$$f = a'b'c + a'bc + ab'c' + abc' + abc$$
$$f = (a + b + c) \cdot (a + b' + c)$$

- (b) Write function  $f$  in short-hand (numerical) notation (both SOP and POS forms).

$$f = \sum m(1, 3, 4, 5, 6, 7)$$
$$f = \prod M(0, 2)$$


(c) Reduce function  $f$  to a minimal form using whatever method you prefer.

$a \ b$		$c$	
		0	1
0	0	0	1
0	1	0	1
1	1	1	1
1	0	1	1


$$f = a + c$$

$$f = a + c$$

 (d) Draw the logic circuit for the minimal form of function  $f$  obtained from part (c) using AND/OR/NOT gates. Make sure to label all wires correctly, including the interior wires. Assume only uncomplemented variables are available.




 (e) Implement  $f$  using only NAND gates. Only uncomplemented inputs are available.




$$f = a + c = \underbrace{(a' \cdot c')}'_{\text{NAND with inverted inputs}}$$

 
(f) Implement  $f$  using only an 8:1 MUX.



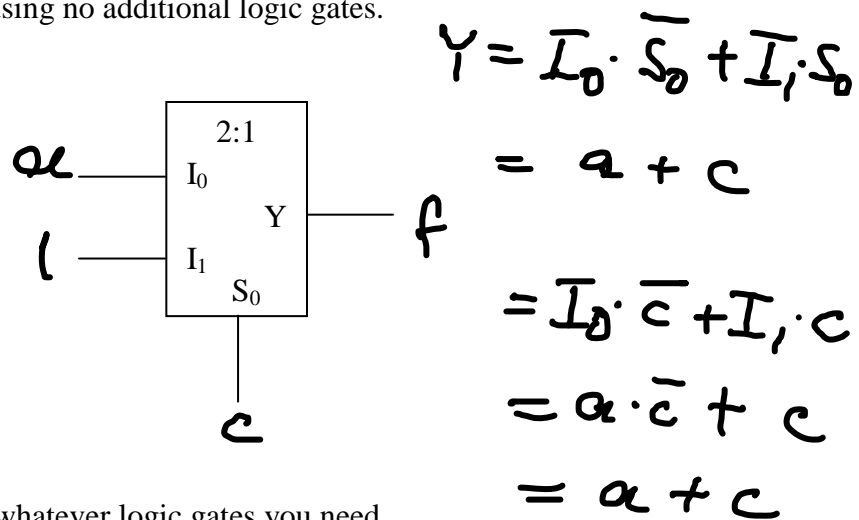
(g) Implement  $f$  using only a 2:1 MUX, using no additional logic gates.



 (h) Implement  $f$  using a 3:8 decoder and whatever logic gates you need.




 - (i) Using the diagram provided, make the appropriate links to implement function  $f$  in a 3-input, 1-output PROM.



Canonical SOP in short-hand

 - (j) Using the diagram provided, make the appropriate links to implement function  $f$  in a 3-input, 1-output PAL.



minimum SOP from part (c)

2. Assume that we have to add two 6-bit numbers in 2's complement form.

(a) Perform the binary addition and indicate if an overflow occurs: (5 points)

leading 1  $\rightarrow$   $\Rightarrow$  neg  
 leading 1  $\rightarrow$   $\Rightarrow$  neg  

$$\begin{array}{r} 100111 \\ + 100110 \\ \hline 1001101 \end{array}$$
 overflow?  $C_{in} = 0$   $\oplus$   $C_{out} = 1$   $\Rightarrow$  overflow

(b) Convert both operands to decimal and add the decimal numbers. Does the result support your finding in (a)? (5 points)

2's complement for both operands

$$\begin{array}{r} 011000 \\ + 011001 \\ \hline 0011001 = 25 \end{array}$$

$$\begin{array}{r} 011001 \\ + 0011010 \\ \hline 0011010 = 26 \end{array}$$

$$\begin{array}{r} -25 \\ + (-26) \\ \hline -51 < -32 \end{array}$$

6 bit:  $-32 \dots +31$   $\downarrow$  overflow

(c) Convert both operands to positive binary numbers using 2's complement arithmetic. Then, convert them to 7-bit numbers by adding a zero on the left side (MSb). Convert them again to negative numbers and perform the binary addition just as in (a). Does the overflow still occur? (5 points)

2's complement of 25 and 26 in 7 bit

$$\begin{array}{r} 1100110 \\ + 1 \\ \hline 1100111 \end{array}$$

$$\begin{array}{r} 1100101 \\ + 1 \\ \hline 1100110 \end{array}$$


$$\begin{array}{r} 1100111 \\ + 1100110 \\ \hline 111001101 \end{array}$$

no overflow


3. Write the decimal number 48 in (a) binary form, (b) hexadecimal form, and (c) octal (base-8) form. (4/3/3 points each, 10 points total)

$48 = 32 + 16 \Rightarrow 0110000_2$   
 3 16  
 6 8

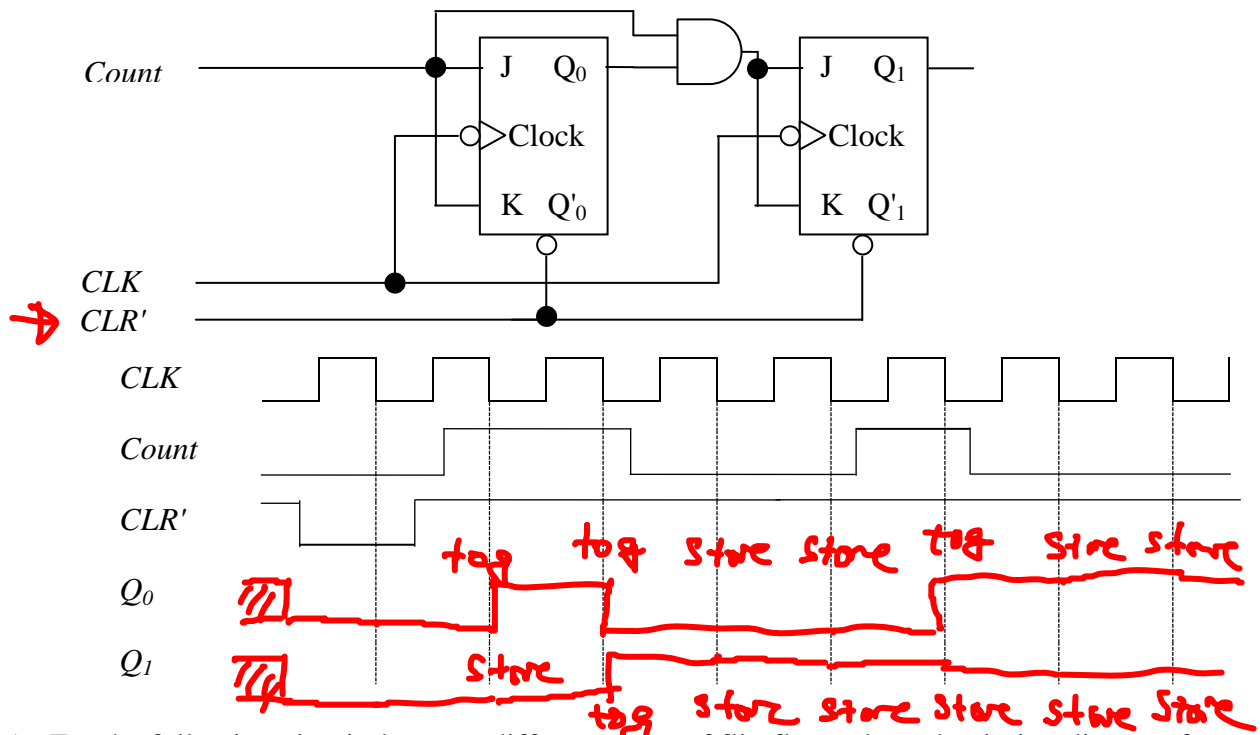4. For the following circuit that uses two  $JK$  flip flops with an active low clear (reset), show the timing diagram for  $Q_0$  and  $Q_1$ . The flip flop is negative-edge triggered, just like the one used in the hardware labs. (10 points).




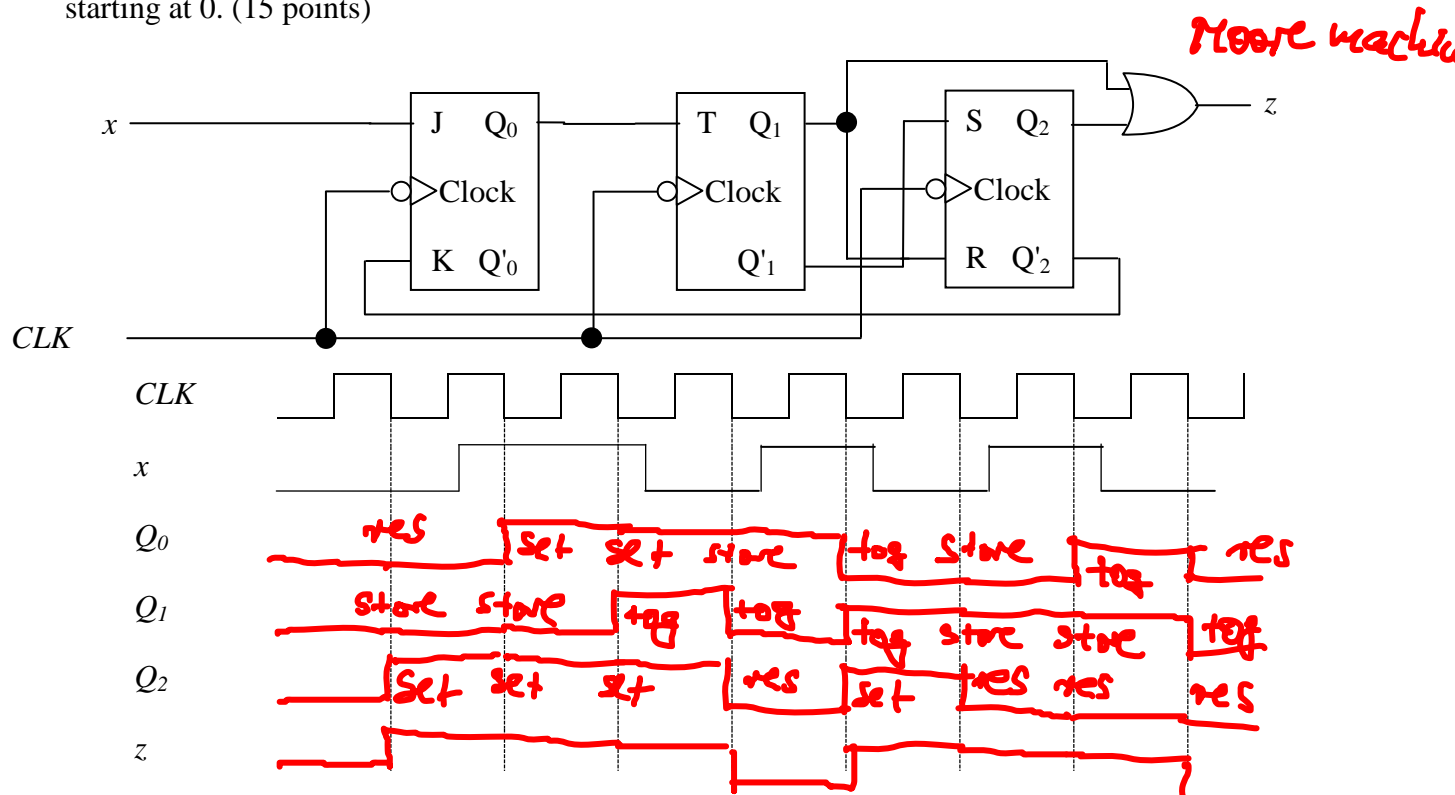5. For the following circuit that uses different types of flip flops, show the timing diagram for the output  $z$ . The flip flops are negative-edge triggered. Assume that all flip flops are initially starting at 0. (15 points)



 6. Design a **synchronous counter** that counts 0, 1, 2, 3, 0, 1, ... (divide-by-4 counter) when an input  $x = 0$ , and counts 0, 1, 2, 0, 1, ... when  $x = 1$  (divide-by-3 counter) using (a) D flip-flops and (b) JK flip-flops.

Note: You need to show the state definition table, the state transition diagram, the state transition table, the K-maps for the respective logic functions and the schematic of the implementation using flip-flops and logic gates in (a) as well as the K-maps for the logic functions and the schematic in (b). (5 points each, 35 points total)




$x$	$q_1$	$q_0$	$q_1^+$	$q_0^+$
0	0	0	0	1
0	0	1	1	0
0	1	0	1	1
0	1	1	0	0
1	0	0	0	1
1	0	1	1	0
1	1	0	0	0
1	1	1	0	0

$x$	$q_1$	$q_0$	$q_1^+$	$q_0^+$
0	0	0	0	1
0	0	1	1	0
1	1	0	0	0
1	0	1	0	1

$$D_1 = x'q_1'q_0' + q_1^+q_0$$

$x$	$q_1$	$q_0$	$q_1^+$	$q_0^+$
0	0	0	0	1
0	0	1	1	0
1	1	0	0	0
1	0	1	0	1

$$D_0 = q_1'q_0' + x'q_0'$$

 

$$J_1 = q_0$$

$$K_1 = x + q_0$$

$$J_0 = q_1' + x'$$

$$K_0 = 1$$

7. Is the following circuit a Moore or a Mealy machine? Explain your answer! (5 points)

